

Chapter 1 Comparison of MOST and bipolar transistors	5
Chapter 2 Amplifiers source followers and cascodes	51
Chapter 3 Differential voltage and current amplifiers	89
Chapter 4 Noise performance of elementary transistor stages	117
Chapter 5 Stability of operational amplifiers	149
Chapter 6 Systematic design of operational amplifiers	181
Chapter 7 Important opamp configurations	211
Chapter 8 Fullydifferential amplifiers	239
Chapter 14 Feedback transimpedance and current amplifiers	389
random and systematic	421
Chapter 16 Bandgap and current reference circuits	457
Chapter 17 Switchedcapacitor filters	485
Chapter 18 Distortion in elementary transistor circuits	519
Chapter 19 Continuoustime filters	567
Chapter 20 CMOS ADC and DAC principles	603
Chapter 21 Lowpower sigmadelta AD converters	637
Chapter 9 Design of multistage operational amplifiers	263
Chapter 10 Currentinput operational amplifiers	291
Chapter 11 Railtorail input and output amplifiers	301
Chapter 12 Class AB and driver amplifiers	337
Chapter 13 Feedback voltage and transconductance amplifiers	363
Chapter 22 Design of crystal oscillators	677
Chapter 23 Lownoise amplifiers	711

Chapter 24 Coupling effects in mixed analogdigital ICs	743
Index of subjects	773

---