

## Contents

Preface	ix
<b>1. The Time and Frequency Domains</b>	<b>1</b>
1.1 Introduction	1
1.2 The Nomenclature of Pulse Techniques	2
1.3 Pulse Spectra	4
1.4 Problems	16
1.5 References	17
1.6 Bibliography	17
<b>2. Transients and Waveshaping in Linear Circuits</b>	<b>18</b>
2.1 Basic Principles	19
2.2 The High-Pass Circuit Model	21
2.3 The Low-Pass Circuit Model	25
2.4 Exponential Inputs—Cascaded Circuits	28
2.5 Attenuators	30
2.6 <i>RLC</i> Circuits	32
2.7 Problems	36
2.8 References	37
<b>3. The Practical Diode Switch</b>	<b>38</b>
3.1 Steady-State Characteristics	38
3.2 Integrated Transistors as Diodes	41
3.3 Transient Characteristics	42
3.4 Charge Control Calculations	45
3.5 Some Practical Diodes	46
3.6 The Schottky Barrier (Hot Carrier) Diode	46
3.7 Reducing Charge Storage Time	49

3.8	Problems	51
3.9	References	52
<b>4.</b>	<b>Diode Clipping and Clamping Circuits</b>	<b>54</b>
4.1	Transfer Characteristics and Clipping	55
4.2	Clipping and Pick-Off Circuits	57
4.3	Clamping and DC Restoration	60
4.4	Problems	64
<b>5.</b>	<b>Pulses on Transmission Lines</b>	<b>66</b>
5.1	Transmission Line Types and Parameters	67
5.2	Matching and Reflections	70
5.3	Inductive and Capacitive Terminations	74
5.4	Losses	76
5.5	Coaxial Cable Response	78
5.6	Microstrip	82
5.7	Non-Uniform Lines	84
5.8	Pulse Generation and Shaping	85
5.9	Problems	87
5.10	References	88
<b>6.</b>	<b>Pulse Transformers</b>	<b>90</b>
6.1	Equivalent Circuits	90
6.2	Rise Time Response	92
6.3	Pulse Top Transmission	95
6.4	Trailing Edge Response	96
6.5	Nonlinear Source and Load Resistance	98
6.6	Effects of Core Materials and Geometry	99
6.7	Transmission Line Transformers	100
6.8	Design Procedures	103
6.9	Problems	105
6.10	References	106

<b>7. Bipolar and Unipolar Transistor Transient Response</b>	<b>107</b>
7.1 Charge Control in the Bipolar Transistor	107
7.1.1 Transition capacitances and delay time	109
7.1.2 Rise time	111
7.1.3 Storage time	115
7.1.4 Fall time	116
7.1.5 Effects of a base speed-up capacitance	116
7.1.6 Provision and measurement of switching parameters	117
7.1.7 A worked example	118
7.2 MOSFET Switching Characteristics	120
7.2.1 The MOSFET with a linear-resistance load	123
7.2.2 Another <i>p</i> -channel MOSFET as load	125
7.2.3 Using a <i>p</i> -channel MOSFET as load with its substrate grounded	128
7.2.4 Using a complementary <i>n</i> -channel MOSFET as load	129
7.3 Problems	130
7.4 References	131
<b>8. Subnanosecond Switching Diodes</b>	<b>133</b>
8.1 The Step-Recovery Diode	133
8.2 The Tunnel (Esaki) Diode	140
8.3 The Gunn Diode	149
8.4 References	153
<b>9. The Characteristics of High-Speed Logic</b>	<b>155</b>
9.1 Transistor-Transistor Logic	156
9.2 Emitter-Coupled Logic	167
9.3 MOS Logic	173
9.4 Integrated Injection Logic	183
9.5 Charge-Coupled Devices	185
9.6 Trends	188
9.7 References	189

<b>10. The Implementation of High-Speed Systems</b>	<b>190</b>
10.1 IC Packaging and Discrete Components	191
10.2 Printed Circuit Boards	193
10.3 The Distribution of Ground, Supplies and Signal Lines	195
10.4 Interconnections	196
10.5 Temperature Effects	205
10.6 References	206
<b>Appendix 1. Additional References</b>	<b>208</b>
<b>Appendix 2. A Selection of Trigonometrical Functions, Integrals and Laplace Transforms</b>	<b>212</b>
<b>Appendix 3. Autocorrelation, Power Spectra and Random Signals</b>	<b>215</b>
<b>Index</b>	<b>217</b>