

Contents

Preface	xiii
Chapter 1. Foundations of Network Theory	1
1. Basic network postulates	2
1.1. Real-time function postulate	3
1.2. Time-invariance postulate	4
1.3. Linearity postulate	5
1.4. Passivity postulate	6
1.5. Causality postulate	9
1.6. Reciprocity postulate	10
2. Matrix characterizations of n -port networks	11
2.1. The impedance matrix	12
2.2. The admittance matrix	13
2.3. The hybrid matrix	14
2.4. The indefinite-admittance matrix	15
3. Power gains	21
4. Hermitian forms	23
5. The positive-real matrix	28
6. Frequency-domain conditions for passivity	39
7. Conclusions	43
Problems	45
References	46
Chapter 2. The Scattering Matrix	48
1. A brief review of the transmission-line theory	49
2. The scattering parameters of a one-port network	50
2.1. Basis-dependent reflection coefficients	52
2.2. Basis-independent reflection coefficient	54
2.3. The factorization of the para-hermitian part of $z(s)$	57

2.4. Alternative representation of the basis-independent reflection coefficient	62
2.5. The normalized reflection coefficient and passivity	64
3. The scattering matrix of an n -port network	66
3.1. Basis-dependent scattering matrices	70
3.2. Basis-independent scattering matrix	74
3.3. The scattering matrices and the augmented n -port networks	77
3.4. Alternative representation of the basis-independent scattering matrix	80
3.5. Physical interpretation of the normalized scattering parameters	82
3.6. The normalized scattering matrix and passivity	88
3.7. The normalized scattering parameters of a lossless two-port network	90
4. The bounded-real scattering matrix	91
5. Interconnection of multi-port networks	98
6. Conclusions	106
Problems	107
References	113
Chapter 3. Approximation and Ladder Realization	115
1. The Butterworth response	116
1.1. Poles of the Butterworth function	118
1.2. Coefficients of the Butterworth polynomials	120
1.3. Butterworth networks	122
1.4. Butterworth LC ladder networks	125
2. The Chebyshev response	132
2.1. Chebyshev polynomials	132
2.2. Equiripple characteristic	134
2.3. Poles of the Chebyshev function	138
2.4. Coefficients of the polynomial $p(y)$	142
2.5. Chebyshev networks	144
2.6. Chebyshev LC ladder networks	146
3. Elliptic functions	152
3.1. Jacobian elliptic functions	152
3.2. Jacobi's imaginary transformations	154

3.3. Periods of elliptic functions	155
3.3.1. The real periods	157
3.3.2. The imaginary periods	158
3.4. Poles and zeros of the Jacobian elliptic functions	159
3.5. Addition theorems and complex arguments	162
4. The elliptic response	165
4.1. The characteristic function $F_n(\omega)$	167
4.2. Equiripple characteristic in passband and stopband	174
A. Maxima and minima in the passband	176
B. Maxima and minima in the stopband	177
C. Transitional band	178
4.3. Poles and zeros of elliptic response	183
4.4. Elliptic networks	190
5. Frequency transformations	196
5.1. Transformation to high-pass	197
5.2. Transformation to band-pass	200
5.3. Transformation to band-elimination	204
6. Conclusions	206
Problems	207
References	215
Chapter 4. Theory of Broadband Matching: The Passive Load	217
1. The Bode-Fano-Youla broadband matching problem	218
2. Youla's theory of broadband matching: preliminary considerations	219
3. Basic constraints on $\rho(s)$	222
4. Bode's parallel RC load	224
4.1. Butterworth transducer power-gain characteristic	225
4.2. Chebyshev transducer power-gain characteristic	235
4.3. Elliptic transducer power-gain characteristic	246
4.4. Equalizer back-end impedance	257
5. Proof of necessity of the basic constraints on $\rho(s)$	259
6. Proof of sufficiency of the basic constraints on $\rho(s)$	264
7. Design procedure for the equalizers	267
8. Darlington type-C load	274
8.1. Butterworth transducer power-gain characteristic	274
8.2. Chebyshev transducer power-gain characteristic	281

CONTENTS

x

8.3. Elliptic transducer power-gain characteristic	287
8.4. Equalizer back-end impedance	290
9. Constant transducer power gain	292
10. Conclusions	306
Problems	307
References	311
Chapter 5. Theory of Broadband Matching: The Active Load	313
1. Special class of active impedances	314
2. General configuration of the negative-resistance amplifiers	316
3. Nonreciprocal amplifiers	319
3.1. Design considerations for N_α	321
3.2. Design considerations for N_β	323
3.3. Design considerations for N_c	324
3.4. Illustrative examples	326
3.4.1. The tunnel diode amplifier: maximally-flat transducer power gain	338
3.4.2. The tunnel diode amplifier: equiripple transducer power gain	346
3.5. Extension and stability	355
4. Transmission-power amplifiers	357
4.1. Tunnel diode in shunt with the load	358
4.1.1. Transducer power gain: $R_2 > R$	359
4.1.2. Transducer power gain: $R_2 < R$	368
4.2. Tunnel diode in shunt with the generator	370
4.2.1. Transducer power gain: $R_1 > R$	372
4.2.2. Transducer power gain: $R_1 < R$	372
4.3. Stability	373
4.4. Sensitivity	375
4.4.1. Tunnel diode in shunt with the load	375
4.4.2. Tunnel diode in shunt with the generator	377
5. Reciprocal amplifiers	378
5.1. General gain-bandwidth limitations	379
5.2. Cascade connection	382
6. Amplifiers using more than one active impedance	388
6.1. Nonreciprocal amplifiers	391

CONTENTS

xi

6.2. Reciprocal amplifiers	394
7. Conclusions	397
Problems	398
References	409
<i>Appendices</i>	
Appendix A. The Butterworth Response	411
Appendix B. The Chebyshev Response	413
Appendix C. The Elliptic Response	417
Symbol index	423
Subject index	427