

Table of Contents

1. **Transistor Amplifiers**
 - Operating principles
 - Common-emitter amplifiers
 - Common-base and common-collector amplifiers
 - Biasing and stabilization
2. **Multistage Amplifiers**
 - Interstage coupling
 - Gain and frequency response
 - Wide-band amplifiers
3. **Power Amplifiers**
 - Class A, B, AB and C amplifiers
 - Push-pull amplifiers
 - Efficiency and distortion
 - Heat dissipation
4. **Field-Effect Transistors**
 - JFETs and MOSFETs
 - Characteristics and biasing
 - FET amplifier circuits
5. **Feedback in Amplifiers**
 - Principles of feedback
 - Effects on gain and stability
 - Positive and negative feedback
6. **Electronic Oscillators**
 - Conditions for oscillation
 - RC, LC and crystal oscillators
 - Signal generation
7. **Operational Amplifiers**
 - Principles and characteristics
 - Inverting and non-inverting circuits
 - Summing amplifiers
 - Integrators and differentiators
 - Comparators
8. **Rectifiers and Power Supplies**
 - Half-wave and full-wave rectification
 - Smoothing filters
 - Voltage regulation
 - Stabilized power supplies
9. **Electronic Switching Devices**
 - Thyristors and controlled devices
 - Switching circuits
 - Electronic control applications
10. **Electronic Circuits and Applications**
 - Signal generation and processing
 - Measurement and control
 - Practical applications of electronic devices