

CONTENTS

Part 1 DC Circuits 1

1 Quantities and Units 3

- 1-1 Scientific and Engineering Notation 4
- 1-2 Units and Metric Prefixes 9
- 1-3 Metric Unit Conversions 11
- 1-4 Measured Numbers 13
- 1-5 Electrical Safety 16

2 Voltage, Current, and Resistance 23

- 2-1 Atoms 24
- 2-2 Electrical Charge 27
- 2-3 Voltage 29
- 2-4 Current 35
- 2-5 Resistance 38
- 2-6 The Electric Circuit 47
- 2-7 Basic Circuit Measurements 54
- Application Assignment: Putting Your Knowledge to Work 61

3 Ohm's Law, Energy, and Power 73

- 3-1 Ohm's Law 74
- 3-2 Application of Ohm's Law 78
- 3-3 Energy and Power 83
- 3-4 Power in an Electric Circuit 86
- 3-5 The Power Rating of Resistors 88
- 3-6 Energy Conversion and Voltage Drop in a Resistance 91
- 3-7 Power Supplies 92
- 3-8 Introduction to Troubleshooting 95
- Application Assignment: Putting Your Knowledge to Work 98

4 Series Circuits 111

- 4-1 Resistors in Series 112
- 4-2 Total Series Resistance 114
- 4-3 Current in a Series Circuit 118
- 4-4 Application of Ohm's Law 120
- 4-5 Voltage Sources in Series 124

- 4-6 Kirchhoff's Voltage Law 127
- 4-7 Voltage Dividers 131
- 4-8 Power in Series Circuits 137
- 4-9 Voltage Measurements 139
- 4-10 Troubleshooting 143
- Application Assignment: Putting Your Knowledge to Work 147

5 Parallel Circuits 165

- 5-1 Resistors in Parallel 166
- 5-2 Total Parallel Resistance 169
- 5-3 Voltage in a Parallel Circuit 174
- 5-4 Application of Ohm's Law 176
- 5-5 Kirchhoff's Current Law 180
- 5-6 Current Dividers 184
- 5-7 Power in Parallel Circuits 188
- 5-8 Troubleshooting 190
- Application Assignment: Putting Your Knowledge to Work 195

6 Series-Parallel Circuits 214

- 6-1 Identifying Series-Parallel Relationships 215
- 6-2 Analysis of Series-Parallel Resistive Circuits 220
- 6-3 Voltage Dividers with Resistive Loads 227
- 6-4 Loading Effect of a Voltmeter 232
- 6-5 The Wheatstone Bridge 234
- 6-6 Thevenin's Theorem 239
- 6-7 The Maximum Power Transfer Theorem 247
- 6-8 The Superposition Theorem 249
- 6-9 Troubleshooting 254
- Application Assignment: Putting Your Knowledge to Work 258

7 Magnetism and Electromagnetism 279

- 7-1 The Magnetic Field 280
- 7-2 Electromagnetism 284
- 7-3 Electromagnetic Devices 290
- 7-4 Magnetic Hysteresis 297
- 7-5 Electromagnetic Induction 299
- 7-6 Applications of Electromagnetic Induction 302
- Application Assignment: Putting Your Knowledge to Work 306

Part 2 AC Circuits 315

8 Introduction to Alternating Current and Voltage 317

- 8-1 The Sinusoidal Waveform 318
- 8-2 Sinusoidal Voltage Sources 323
- 8-3 Voltage and Current Values of Sine Waves 327
- 8-4 Angular Measurement of a Sine Wave 330
- 8-5 The Sine Wave Formula 334
- 8-6 Analysis of AC Circuits 338
- 8-7 Superimposed DC and AC Voltages 340
- 8-8 Nonsinusoidal Waveforms 342
- 8-9 The Oscilloscope 349
- Application Assignment: Putting Your Knowledge to Work 356

9 Capacitors 373

- 9-1 The Basic Capacitor 374
- 9-2 Types of Capacitors 381
- 9-3 Series Capacitors 386
- 9-4 Parallel Capacitors 390
- 9-5 Capacitors in DC Circuits 392
- 9-6 Capacitors in AC Circuits 401
- 9-7 Capacitor Applications 406
- Application Assignment: Putting Your Knowledge to Work 411

10 RC Circuits 425

- 10-1 Sinusoidal Response of RC Circuits 426
- 10-2 Impedance and Phase Angle of Series RC Circuits 427
- 10-3 Analysis of Series RC Circuits 429
- 10-4 Impedance and Phase Angle of Parallel RC Circuits 440
- 10-5 Analysis of Parallel RC Circuits 443
- 10-6 Analysis of Series-Parallel RC Circuits 447
- 10-7 Power in RC Circuits 452
- 10-8 Basic Applications 456
- 10-9 Troubleshooting 462
- Application Assignment: Putting Your Knowledge to Work 467

11 Inductors 482

- 11-1 The Basic Inductor 483
- 11-2 Types of Inductors 488
- 11-3 Series and Parallel Inductors 489
- 11-4 Inductors in DC Circuits 491
- 11-5 Inductors in AC Circuits 501
- 11-6 Inductor Applications 506
- Application Assignment: Putting Your Knowledge to Work 508

12 RL Circuits 518

- 12-1 Sinusoidal Response of RL Circuits 519
- 12-2 Impedance and Phase Angle of Series RL Circuits 520
- 12-3 Analysis of Series RL Circuits 522
- 12-4 Impedance and Phase Angle of Parallel RL Circuits 531
- 12-5 Analysis of Parallel RL Circuits 534
- 12-6 Analysis of Series-Parallel RL Circuits 536
- 12-7 Power in RL Circuits 540
- 12-8 Basic Applications 543
- 12-9 Troubleshooting 546
- Application Assignment: Putting Your Knowledge to Work 550

13 RLC Circuits and Resonance 563

- 13-1 Impedance and Phase Angle of Series RLC Circuits 564
- 13-2 Analysis of Series RLC Circuits 565
- 13-3 Series Resonance 570
- 13-4 Series Resonant Filters 577
- 13-5 Parallel RLC Circuits 585
- 13-6 Parallel Resonance 590
- 13-7 Parallel Resonant Filters 598
- 13-8 Applications 603
- Application Assignment: Putting Your Knowledge to Work 607

14 Transformers 616

- 14-1 Mutual Inductance 617
- 14-2 The Basic Transformer 618
- 14-3 Step-Up and Step-Down Transformers 622
- 14-4 Loading the Secondary 625
- 14-5 Reflected Load 627
- 14-6 Impedance Matching 629
- 14-7 Nonideal Transformer Characteristics 632
- 14-8 Tapped and Multiple-Winding Transformers 635
- 14-9 Troubleshooting 638
- Application Assignment: Putting Your Knowledge to Work 640

15 Time Response of Reactive Circuits 652

- 15-1 The RC Integrator 653
- 15-2 Response of RC Integrators to a Single Pulse 654
- 15-3 Response of RC Integrators to Repetitive Pulses 659
- 15-4 Response of RC Differentiators to a Single Pulse 663
- 15-5 Response of RC Differentiators to Repetitive Pulses 668
- 15-6 Response of RL Integrators to Pulse Inputs 670

- 15-7 Response of *RL* Differentiators to Pulse Inputs 675
- 15-8 Applications 678
- 15-9 Troubleshooting 681
- Application Assignment: Putting Your Knowledge to Work 683

Part 3 Devices 693

16 Diodes and Applications 695

- 16-1 Introduction to Semiconductors 696
- 16-2 The Diode 702
- 16-3 Diode Characteristics 707
- 16-4 Diode Rectifiers 711
- 16-5 Power Supplies 719
- 16-6 Special-Purpose Diodes 725
- 16-7 Troubleshooting 733
- Application Assignment: Putting Your Knowledge to Work 739

17 Transistors and Applications 754

- 17-1 DC Operation of Bipolar Junction Transistors (BJTs) 755
- 17-2 BJT Class A Amplifiers 759
- 17-3 BJT Class B Amplifiers 772
- 17-4 The BJT as a Switch 778
- 17-5 DC Operations of Field-Effect Transistors (FETs) 780
- 17-6 FET Amplifiers 788
- 17-7 Feedback Oscillators 793
- 17-8 Troubleshooting 799
- Application Assignment: Putting Your Knowledge to Work 803

18 The Operational Amplifier 818

- 18-1 Introduction to the Operational Amplifier 819
- 18-2 The Differential Amplifier 821
- 18-3 Op-Amp Parameters 827
- 18-4 Negative Feedback 833
- 18-5 Op-Amp Configurations with Negative Feedback 835
- 18-6 Op-Amp Impedances 840
- 18-7 Troubleshooting 843
- Application Assignment: Putting Your Knowledge to Work 846

19 Basic Op-Amp Circuits 857

- 19-1 Comparators 858
- 19-2 Summing Amplifiers 861
- 19-3 Integrators and Differentiators 865
- 19-4 Oscillators 871
- 19-5 Active Filters 877
- 19-6 Voltage Regulators 885
- Application Assignment: Putting Your Knowledge to Work 893

20 Special-Purpose Op-Amp Circuits 904

- 20-1 Instrumentation Amplifiers 905
- 20-2 Isolation Amplifiers 909
- 20-3 Operational Transconductance Amplifiers (OTAs) 914
- 20-4 Active Diode Circuits 921
- 20-5 Current Sources and Converters 927
- Application Assignment: Putting Your Knowledge to Work 929

21 Measurement, Conversion, and Control 942

- 21-1 Temperature Measurement 943
- 21-2 Strain, Pressure, and Flow Rate Measurements 952
- 21-3 Motion Measurement 957
- 21-4 Sample-and-Hold Circuits 960
- 21-5 Analog-to-Digital Conversion 963
- 21-6 Power-Control Circuits 968
- Application Assignment: Putting Your Knowledge to Work 972

APPENDICES

- A** Table of Standard Resistor Values 983
- B** Capacitor Color Coding and Marking 984
- C** Norton's Theorem and Millman's Theorem 988
- D** Devices Data Sheets 993
- E** Field-Programmable Analog Arrays (FPAAs) 1003

Answers to Odd-Numbered Problems 1012

Glossary 1025

Index 1034