
CONTENTS

Preface	xi
1 Operational Amplifier Fundamentals	1
1.1 Amplifier Fundamentals	2
1.2 The Operational Amplifier	5
1.3 Basic Op Amp Configurations	8
1.4 Ideal Op Amp Circuit Analysis	15
1.5 Negative Feedback	23
1.6 Feedback in Op Amp Circuits	29
1.7 The Loop Gain	37
1.8 Op Amp Powering	41
Problems	47
Bibliography	58
Appendix 1A Standard Resistor Values	58
2 Circuits with Resistive Feedback	60
2.1 Current-to-Voltage Converters	61
2.2 Voltage-to-Current Converters	63
2.3 Current Amplifiers	71
2.4 Difference Amplifiers	73
2.5 Instrumentation Amplifiers	79
2.6 Instrumentation Applications	86
2.7 Transducer Bridge Amplifiers	91
Problems	98
References	105
3 Active Filters: Part I	106
3.1 The Transfer Function	109
3.2 First-Order Active Filters	115
3.3 Audio Filter Applications	121
3.4 Standard Second-Order Responses	126
3.5 <i>KRC</i> Filters	133
3.6 Multiple-Feedback Filters	141
3.7 State-Variable and Biquad Filters	144
3.8 Sensitivity	150
Problems	153
References	158
4 Active Filters: Part II	160
4.1 Filter Approximations	161
4.2 Cascade Design	166
4.3 Generalized Impedance Converters	175
4.4 Direct Design	181

4.5	The Switched Capacitor	187
4.6	Switched-Capacitor Filters	192
4.7	Universal SC Filters	198
	Problems	204
	References	210
5	Static Op Amp Limitations	211
5.1	Simplified Op Amp Circuit Diagram	212
5.2	Input Bias and Offset Currents	217
5.3	Low-Input-Bias-Current Op Amps	221
5.4	Input Offset Voltage	225
5.5	Low-Input-Offset-Voltage Op Amps	230
5.6	Input Offset-Error Compensation	235
5.7	Maximum Ratings	240
	Problems	244
	References	248
	Appendix 5A Data Sheets of the μ A741 Op Amp	249
6	Dynamic Op Amp Limitations	258
6.1	Open-Loop Response	259
6.2	Closed-Loop Response	263
6.3	Input and Output Impedances	269
6.4	Transient Response	275
6.5	Effect of Finite GBP on Integrator Circuits	283
6.6	Effect of Finite GBP on Filters	289
6.7	Current-Feedback Amplifiers	293
	Problems	303
	References	309
7	Noise	311
7.1	Noise Properties	313
7.2	Noise Dynamics	317
7.3	Sources of Noise	322
7.4	Op Amp Noise	328
7.5	Noise in Photodiode Amplifiers	335
7.6	Low-Noise Op Amps	339
	Problems	342
	References	346
8	Stability	347
8.1	The Stability Problem	348
8.2	Stability in Constant-GBP Op Amp Circuits	356
8.3	Internal Frequency Compensation	365
8.4	External Frequency Compensation	374
8.5	Stability in CFA Circuits	381
8.6	Composite Amplifiers	384
	Problems	390
	References	396
9	Nonlinear Circuits	398
9.1	Voltage Comparators	399
9.2	Comparator Applications	407

9.3	Schmitt Triggers	416
9.4	Precision Rectifiers	422
9.5	Analog Switches	428
9.6	Peak Detectors	433
9.7	Sample-and-Hold Amplifiers	437
	Problems	443
	References	448
10	Signal Generators	449
10.1	Sine Wave Generators	451
10.2	Multivibrators	457
10.3	Monolithic Timers	463
10.4	Triangular Wave Generators	471
10.5	Sawtooth Wave Generators	478
10.6	Monolithic Waveform Generators	478
10.7	V-F and F-V Converters	480
	Problems	492
	References	497
11	Voltage References and Regulators	499
11.1	Performance Specifications	500
11.2	Voltage References	508
11.3	Voltage-Reference Applications	512
11.4	Linear Regulators	519
11.5	Linear-Regulator Applications	527
11.6	Switching Regulators	533
11.7	Monolithic Switching Regulators	544
	Problems	551
	References	557
12	D-A and A-D Converters	559
12.1	Performance Specifications	561
12.2	D-A Conversion Techniques	567
12.3	Multiplying DAC Applications	580
12.4	A-D Conversion Techniques	584
12.5	Oversampling Converters	593
	Problems	601
	References	606
13	Nonlinear Amplifiers and Phase-Locked Loops	607
13.1	Log/Antilog Amplifiers	608
13.2	Analog Multipliers	613
13.3	Operational Transconductance Amplifiers	620
13.4	Phase-Locked Loops	627
13.5	Monolithic PLLs	633
	Problems	642
	References	646
	Index	647