



Contents / v

Preface / ix

Section I Devices and Op-Amps / 1

Chapter 1 Introduction to Diodes / 3

- 1.1 Introduction to Diodes / 4
- 1.2 Inside the Diode / 6
- 1.3 Three Diode Models / 10
- 1.4 Computer Circuit Analysis / 16
- 1.5 MultiSIM Lab Exercise / 17

Chapter 2 Diode Circuits / 35

- 2.1 Rectifier Circuits / 35
- 2.2 Filtering Pulsating DC / 40
- 2.3 Block Diagram of a Complete Power Supply System / 42
- 2.4 Voltage Multipliers / 42
- 2.5 Clipper Circuits / 43
- 2.6 Clamper Circuits / 47
- 2.7 Diode Switching Circuits / 50
- 2.8 Diode Characteristics and Data Sheets / 51
- 2.9 Troubleshooting Diodes / 51
- Pre-Lab 2.1 Diode Rectifier Circuits / 55
- Lab 2.1 Diode Rectifier Circuits / 57
- Pre-Lab 2.2 Clipper and Clamper Circuits / 61
- Lab 2.2 Clipper and Clamper Circuits / 63

Chapter 3 Special Diodes / 77

- 3.1 Zener Diodes / 77
- 3.2 Zener Diode Applications / 78
- 3.3 Voltage Surge Protectors / 83
- 3.4 Varactor Diodes / 84
- 3.5 High Frequency Switching Diodes / 86
- 3.6 Light-Emitting Diodes (LEDs) / 88
- 3.7 Photodiodes / 91
- 3.8 Troubleshooting Special Diodes / 92
- Pre-Lab 3.1 Zener Diode Voltage Regulator Circuit / 95
- Lab 3.1 Zener Diode Voltage Regulator Circuit / 97
- Pre-Lab 3.2 LED Circuits / 99
- Lab 3.2 LED Circuits / 101

Chapter 4 The Bipolar Transistor / 113

- 4.1 Introduction to Transistors / 113
- 4.2 Inside the Transistor / 114
- 4.3 Transistor Switches / 118
- 4.4 Transistor Characteristics and Data Sheets / 122
- 4.5 The Transistor Amplifier / 123
- 4.6 Signal Analysis of the Base-Biased Amplifier / 127
- 4.7 Measuring Input and Output Impedance / 134
- 4.8 Transistor Output Characteristic Curves / 136

- 4.9 Troubleshooting Transistors / 139
- Pre-Lab 4.1 Transistor Switch and Transistor Amplifier / 143
- Lab 4.1 Transistor Switch and Transistor Amplifier / 145

Chapter 5 Transistor Circuits / 161

- 5.1 Introduction / 161
- 5.2 Voltage Divider Biasing / 164
- 5.3 Signal Parameters in Voltage Divider Circuits / 166
- 5.4 Variations of Voltage Divider Biased Amplifiers / 170
- 5.5 Emitter Biased Amplifier / 175
- 5.6 Voltage-Mode Feedback Biased Amplifier / 177
- 5.7 Multistage RC Coupled Amplifiers / 178
- 5.8 Coupling and Bypass Capacitors / 179
- 5.9 Direct Coupled Amplifiers / 181
- 5.10 Troubleshooting Transistor Circuits / 183
- Pre-Lab 5.1 Voltage Divider Biased Amplifiers / 185
- Lab 5.1 Voltage Divider Biased Amplifiers / 187
- Pre-Lab 5.2 Multistage Amplifier / 189
- Lab 5.2 Multistage Amplifier / 191

Chapter 6 Other Transistor Circuits / 203

- 6.1 Common-Collector Amplifiers / 203
- 6.2 Power and Current Gain / 207
- 6.3 Darlington Pairs / 209
- 6.4 Common-Collector Stage in the Multistage Amplifier / 211
- 6.5 Common-Base Amplifiers / 212
- 6.6 Comparison of Amplifier Configurations / 214
- 6.7 Current Sources / 215
- 6.8 Differential Amplifiers / 217
- 6.9 Troubleshooting Other Transistor Circuits / 220
- Pre-Lab 6.1 Emitter Follower Buffer / 223
- Lab 6.1 Emitter Follower Buffer / 225

Chapter 7 Junction Field Effect Transistors / 239

- 7.1 Introduction to JFETs / 239
- 7.2 The JFET Versus the Bipolar Transistor / 241
- 7.3 JFET Characteristics / 241
- 7.4 Biasing the Common-Source JFET Amplifier / 246
- 7.5 JFET Signal Parameters / 252

- 7.6 Analyzing JFET Amplifier Circuits / 255
- 7.7 Common-Drain Amplifier / 259
- 7.8 N-Channel and P-Channel JFETs / 263
- 7.9 JFET Switching Circuits / 264
- 7.10 Troubleshooting JFET Circuits / 265
- Pre-Lab 7.1 JFET Amplifiers / 267
- Lab 7.1 JFET Amplifiers / 279

Chapter 8 MOSFETs / 283

- 8.1 Introduction to MOSFETs / 283
- 8.2 D-MOSFET / 283
- 8.3 E-MOSFET / 286
- 8.4 Handling MOSFETs / 290
- 8.5 MOSFET Parameters / 291
- 8.6 MOSFET Applications / 292
- 8.7 Troubleshooting FET Circuits / 297
- Pre-Lab 8.1 MOSFET Amplifier and Switching Circuits / 303
- Lab 8.1 MOSFET Amplifier and Switching Circuits / 305

Chapter 9 Basics of Operational Amplifiers / 317

- 9.1 Introduction to Op-Amps / 317
- 9.2 Voltage Follower / 319
- 9.3 Noninverting Amplifier / 320
- 9.4 Inside the Op-Amp and Negative Feedback / 322
- 9.5 The Inverting Amplifier / 325
- 9.6 Comparators / 326
- 9.7 Troubleshooting Op-Amp Circuits / 328
- Pre-Lab 9.1 Basic Op-Amp Circuits / 329
- Lab 9.1 Basic Op-Amp Circuits / 331

Chapter 10 Op-Amp Limitations / 343

- 10.1 Input Bias Current / 343
- 10.2 Input Offset Current / 344
- 10.3 Input Offset Voltage / 345
- 10.4 Output Voltage Swing / 347
- 10.5 Output Short-Circuit Current / 348
- 10.6 Frequency Response / 349
- 10.7 Working with Logarithmic Scales / 356
- 10.8 Slew Rate (SR) / 359
- 10.9 Troubleshooting IC Op-Amp Circuits / 365
- Pre-Lab 10.1 Op-Amp Limitations / 367
- Lab 10.1 Op-Amp Limitations / 371

Section II Subsystems / 391

Chapter 11 Op-Amp Applications / 395

- 11.1 High Input Impedance Circuits / 395
- 11.2 Basic Arithmetic Circuits / 397

- 11.3 Mixers and Periodic Signals / 400
- 11.4 Integration / 402
- 11.5 Differentiation / 405
- 11.6 Single Supply Op-Amp Circuits / 407
- 11.7 Precision Rectifier Circuits / 408
- 11.8 Peak Detector / 410
- 11.9 Comparator Circuits / 411
- 11.10 Troubleshooting Op-Amp Applications / 417
- Pre-Lab 11.1 Pulse-Activated Switching System / 419
- Lab 11.1 Sound-Activated Switching System / 421
- Chapter 12 Filter Circuits / 439**
- 12.1 Introduction to Filter Circuits / 439
- 12.2 Passive RC Filter Circuits / 440
- 12.3 Roll-Off / 443
- 12.4 Bode Plot / 444
- 12.5 First-Order Active Filters / 445
- 12.6 Higher-Order Active Filters / 446
- 12.7 Bandpass Filters / 448
- 12.8 Bandstop Filters / 452
- 12.9 State-Variable Filters / 453
- 12.10 Switched Capacitor Filters / 454
- 12.11 LC Tuned Amplifier / 455
- 12.12 Crystal and Other Piezoelectric Filters / 457
- 12.13 Troubleshooting Filter Circuits / 459
- Pre-Lab 12.1 Active RC Filters / 461
- Lab 12.1 Active RC Filters / 465
- Chapter 13 Sine Wave Oscillator Circuits / 483**
- 13.1 Introduction to Basic Oscillator Theory / 483
- 13.2 RC Sine Wave Oscillator Circuits / 484
- 13.3 Oscillations in Amplifier Circuits / 488
- 13.4 LC Oscillator Circuits / 489
- 13.5 Crystal Oscillator Circuits / 491
- 13.6 Troubleshooting Sine Wave Oscillator Circuits / 493
- Pre-Lab 13.1 Sine Wave Oscillators / 495
- Lab 13.1 Sine Wave Oscillators / 497
- Chapter 14 Nonsinusoidal Oscillators / 511**
- 14.1 Introduction to Rectangular Wave Oscillators / 511
- 14.2 The 555 Astable Circuit / 512
- 14.3 The 555 as a Monostable Circuit / 516
- 14.4 Inverter Oscillators / 518
- 14.5 Schmitt Trigger RC Oscillators / 519
- 14.6 Crystal Controlled Oscillators / 521
- 14.7 Triangular Wave Oscillators / 521
- 14.8 Wave Shaping a Triangular Wave into a Sine Wave / 525
- 14.9 Sawtooth Oscillators / 526
- 14.10 Troubleshooting Oscillator Circuits / 528
- Pre-Lab 14.1 Periodic Waveform Oscillators / 529
- Lab 14.1 Periodic Waveform Oscillators / 533
- Chapter 15 Special ICs / 547**
- 15.1 Differential Amplifiers / 547
- 15.2 Instrumentation Amplifiers / 553
- 15.3 Operational Transconductance Amplifiers (OTAs) / 555
- 15.4 Optoisolators / 557
- 15.5 Voltage-Controlled Oscillators (VCOs) / 559
- 15.6 Phase-Locked Loop (PLL) / 561
- 15.7 PLL Applications / 564
- 15.8 Troubleshooting ICs / 566
- Pre-Lab 15.1 Differential Amplifier and PLL Circuit / 567
- Lab 15.1 Differential Amplifier and PLL Circuit / 569
- Chapter 16 Power Circuits: Switching and Amplifying / 585**
- 16.1 Introduction to Power Circuits / 585
- 16.2 Power MOSFETs Versus Power Bipolar Transistors / 588
- 16.3 Power Switching Circuits / 591
- 16.4 Classes of Amplifiers / 593
- 16.5 Class-C Power Amplifiers / 596
- 16.6 Class-B Power Amplifiers / 596
- 16.7 Integrated Power Amplifiers / 602
- 16.8 Class-D Power Amplifiers / 603
- 16.9 Heat Sinking Power Devices / 604
- 16.10 Troubleshooting Power Circuits / 606
- Pre-Lab 16.1 Power Amplifiers / 607
- Lab 16.1 Power Amplifiers / 609
- Chapter 17 Thyristors / 623**
- 17.1 Introduction to Thyristors / 623
- 17.2 Silicon-Controlled Rectifiers (SCRs) / 623
- 17.3 Triacs / 628
- 17.4 Gate-Turnoff SCR (GTO) / 629
- 17.5 Silicon-Controlled Switch (SCS) / 630
- 17.6 Shockley Diode / 630
- 17.7 Diacs / 631
- 17.8 Unijunction Transistors (UJTs) / 631
- 17.9 Programmable Unijunction Transistor (PUT) / 635
- 17.10 SCR Phase-Control Circuits / 636

- 17.11 Triac Phase-Control Circuits / 637
 17.12 MOS-Gated Thyristors / 639
 17.13 Troubleshooting Thyristor Circuits / 640
 Pre-Lab 17.1 SCR Phase Control / 641
 Lab 17.1 SCR Phase Control / 643
 Pre-Lab 17.2 Triac Phase Control / 647
 Lab 17.2 Triac Phase Control / 649
- Chapter 18 Power Supplies / 663
- 18.1 Introduction to Power Supplies / 663
 18.2 Linear Versus Switching Power Supplies / 666
 18.3 Linear Power Supplies / 669
 18.4 IC Linear Regulators / 674
 18.5 Switching Regulators / 678
 18.6 IC Regulators / 685
 18.7 Troubleshooting Power Supplies / 689
 Pre-Lab 18.1 Linear Regulated Power Supply / 691
 Lab 18.1 Linear Regulated Power Supply / 693
 Pre-Lab 18.2 Switching Regulators / 697
 Lab 18.2 Switching Regulators / 699
- Chapter 19 Data Conversion / 715
- 19.1 Introduction to Data Conversion Systems / 715
 19.2 Relationship Between Analog and Digital Signals / 716
 19.3 Resolution of Conversion Systems / 718
 19.4 Digital-to-Analog Conversion / 720
 19.5 Integrated DAC / 722
 19.6 Digital Controlled Amplifier / 723
 19.7 Analog-to-Digital Conversion / 724
 19.8 Integrated ADC / 727
 19.9 Sample-and-Hold Circuit / 728
 19.10 Troubleshooting Conversion Systems / 729
 Pre-Lab 19.1 ADC and DAC / 731
 Lab 19.1 ADC and DAC / 733
- Chapter 20 Optoelectronics / 743
- 20.1 Introduction to Optoelectronics / 743
 20.2 Cathode Ray Tubes (CRTs) / 743
 20.3 Liquid-Crystal Displays (LCDs) / 748
 20.4 LEDs / 750
 20.5 Light Sensing Devices / 751
 20.6 Photoactive Devices / 753
 20.7 Optoisolators and Optical Sensors / 756
 20.8 Lasers / 757
 20.9 Laser Diodes / 759
 20.10 Fiber Optics / 760
 Pre-Lab 20.1 Optical Sensors and Optoisolators / 767
 Lab 20.1 Optical Sensors and Optoisolators / 769
- Chapter 21 Transducers and Actuators / 781
- 21.1 Introduction to Transducers and Actuators / 781
 21.2 Temperature Sensors / 782
 21.3 Displacement Sensors / 790
 21.4 Pressure Transducers / 794
 21.5 Flow Transducers / 795
 21.6 Acceleration Sensors / 796
 21.7 Magnetic Sensors / 797
 21.8 Sensor Signal Conditioning and Calibration / 801
 21.9 Solenoids / 802
 21.10 Relays / 803
 21.11 Motors / 804
 21.12 Speakers / 814
 Pre-Lab 21.1 Fan Control System / 815
 Lab 21.1 Fan Control System / 817
- Appendix A Components List / 833
- Appendix B Components Data / 837
- Appendix C Answers to Odd-Numbered Questions and Problems / 859
- Index / 875