

# TABLE OF CONTENTS

## PART 1: DC CIRCUITS

### Chapter 1: Quantities and Units

- Scientific and engineering notation
- Units and metric prefixes
- Metric unit conversions
- Measured numbers
- Electrical safety

### Chapter 2: Voltage, Current, and Resistance

- Atoms and structure of matter
- Electrical charge
- Voltage (potential difference)
- Current
- Resistance
- The electric circuit
- Basic circuit measurements

### Chapter 3: Ohm's Law, Energy, and Power

- Ohm's law
- Applications of Ohm's law
- Energy and power
- Power in electric circuits
- Power rating of resistors
- Voltage drops and energy conversion
- Power supplies
- Introduction to troubleshooting

### Chapter 4: Series Circuits

- Resistors in series
- Total resistance
- Current in series circuits
- Voltage sources in series
- Kirchhoff's Voltage Law (KVL)
- Voltage dividers
- Power in series circuits
- Voltage measurements

## **Chapter 5: Parallel Circuits**

- Resistors in parallel
- Total parallel resistance
- Current distribution
- Kirchhoff's Current Law (KCL)
- Current dividers
- Power in parallel circuits

## **Chapter 6: Series-Parallel Circuits**

- Circuit analysis techniques
- Voltage and current calculations
- Loading effects
- Network simplification

## **Chapter 7: Magnetism and Electromagnetism**

- Magnetic fields
- Electromagnetism
- Induction principles
- Relays and electromagnetic devices

# **PART 2: AC CIRCUITS**

## **Chapter 8: Introduction to Alternating Current and Voltage**

- AC waveforms
- Frequency and period
- Phase relationships
- RMS values

## **Chapter 9: Capacitors**

- Capacitance and dielectric materials
- Charging and discharging
- Types of capacitors
- Capacitors in series and parallel

## **Chapter 10: RC Circuits**

- Time constants
- Transient response
- RC filters

## **Chapter 11: Inductors**

- Inductance
- Magnetic coupling
- Energy storage

## **Chapter 12: RL Circuits**

- RL transient response
- Time constant

## **Chapter 13: RLC Circuits and Resonance**

- Series and parallel resonance
- Quality factor (Q)
- Bandwidth

## **Chapter 14: Transformers**

- Transformer operation
- Turns ratio
- Power transfer
- Types of transformers

## **Chapter 15: Time Response of Reactive Circuits**

- Transient analysis
- Exponential behavior
- Switching circuits

# **PART 3: DEVICES**

## **Chapter 16: Diodes and Applications**

- Semiconductor theory
- PN junction
- Rectifiers
- Zener diodes
- Diode applications

## **Chapter 17: Transistors and Applications**

- BJT operation
- Biasing
- Amplification
- Switching

## **Chapter 18: The Operational Amplifier**

- Op-amp basics
- Ideal vs practical characteristics

## **Chapter 19: Basic Op-Amp Circuits**

- Inverting amplifier
- Non-inverting amplifier
- Voltage follower

## **Chapter 20: Special-Purpose Op-Amp Circuits**

- Integrators and differentiators
- Comparators
- Active filters

## **Chapter 21: Measurement, Conversion, and Control**

- Sensors and transducers
- Analog-to-digital conversion
- Digital-to-analog conversion
- Control systems