

Contents

Chapter-1: Semiconductor Materials and Properties	1-43
1.1 Introduction	2
1.2 Energy Bands	2
1.3 Insulators, Conductors and Semiconductors	5
1.4 Semiconductor Current	13
1.5 Donor and Acceptor Impurities	15
1.6 Doping	17
1.7 Fermi Level	22
1.8 The Mass-Action Law	24
1.9 Mobility	26
1.10 Diffusion	32
<i>Self Test</i>	34
<i>Solved Examples</i>	35
Chapter-2: Junction Diode and Diode Applications	44-159
2.1 Introduction	45
2.2 p-n Junction	45
2.3 V-I Characteristics of a pn-Junction Diode	53
2.4 Static and Dynamic Resistance of a pn-Junction Diode	57
2.5 Diode Capacitance	58
2.6 Different Ratings of Diode	61
<i>Self Test</i>	61
<i>Solved Examples</i>	62
2.7 Introduction to Diode Rectifier	75
<i>Self Test</i>	85
<i>Solved Examples</i>	86
2.8 Full-Wave Rectifier (FWR)	98
2.9 FWR with Center Tapped Transformer	98
2.10 Full-Wave Bridge Rectifier	107
2.11 Comparison of Rectifier Circuit	109

	<i>Self Test</i>	110
	<i>Solved Examples</i>	110
2.12	Filters	123
	<i>Self Test</i>	129
	<i>Solved Examples</i>	129
2.13	Clipping Circuits	132
2.14	Clamper Circuits	146
	<i>Self Test</i>	149
	<i>Solved Examples</i>	150
Chapter-3: Special Diodes		160-189
3.1	Introduction	161
3.2	Zener Diode (Breakdown Mechanism)	161
3.3	Breakdown Characteristic of a Zener Diode	164
3.4	Zener Resistance	164
3.5	Zener Diode Specification	165
3.6	Zener Diode Application as a Shunt Regulator	166
3.7	Light-Emitting Diode	167
3.8	Schottky Diode	171
	<i>Self Test</i>	174
	<i>Solved Examples</i>	174
Chapter-4: Bipolar Junction Transistor		190-291
4.1	Introduction	191
4.2	Transistor	191
4.3	Different Types of Transistor Configuration	201
4.4	Transistor as a Switch	202
4.5	Characteristics of BJT	206
4.6	Operating Point	218
4.7	Stabilization	221
4.8	Transistor Biasing	235
	<i>Solved Examples</i>	246
	<i>Self test</i>	291
Chapter-5: BJT as an Amplifier		292-325
5.1	Introduction	293
5.2	Classification of Amplifiers	293

5.3	Hybrid Parameter (h-Parameter) Model	295
	<i>Solved Examples</i>	316
	<i>Self test</i>	324
Chapter-6: Field Effect Transistors (FETs) & Mosfets		326-380
6.1	Introduction to FET	327
6.2	Structure of JFET or FET	329
6.3	Introduction to MOSFET	350
6.4	Structure and Operation of a Enhancement Type MOSFET	350
6.5	Structure and Operation of a Depletion Type MOSFET	356
6.6	Circuit Symbols for FET and MOSFET	359
6.7	Comparison of FET and MOSFET	359
6.8	Biasing in MOS Amplifier Circuits	360
	<i>Solved Examples</i>	370
Chapter-7: Operational Amplifiers		381-441
7.1	Introduction	382
7.2	Basics of Operational Amplifier	382
7.3	Basic Circuit Symbol	382
7.4	Packages	383
7.5	Schematic Symbol	385
7.6	Block Diagram of Operational Amplifier	385
7.7	Ideal Operational Amplifier	386
7.8	Equivalent Circuit of Operational Amplifier	387
7.9	Need of Feedback	388
7.10	Inverting Amplifier	389
	<i>Self Test</i>	392
	<i>Solved Examples</i>	393
7.11	Non-Inverting Amplifier	395
	<i>Self Test</i>	397
	<i>Solved Examples</i>	398
7.12	Operational Amplifier Applications	401
	<i>Self Test</i>	410
	<i>Solved Examples</i>	411
	<i>Miscellaneous Examples</i>	414
Chapter-8: Switching Theory & Logic Design		442-554
8.1	Introduction	443
8.2	Logic Levels and Pulse Waveforms	443

8.3	Number System	444
8.4	Conversion of Bases	446
8.5	Binary Codes	454
8.6	Non-weighted Codes	458
8.7	Complements	460
8.8	Logic Gates	468
8.9	Combination of Basic Logic Gates and Universal Gates	471
8.10	Boolean Algebra	476
8.11	Simplification of Boolean Function using Truth Table	493
8.12	Conversion of AND/OR/NOT Logic to NAND/ NOR Logic	509
	<i>Self Test</i>	510
	<i>Solved Examples</i>	511
Chapter-9: Electronics Instruments		555-584
9.1	Introduction to Cathode Ray Tube (CRT)	556
9.2	Introduction to Cathode Ray Oscilloscope (CRO)	556
9.3	Principles and Operation of an Oscilloscope	556
9.4	Block Diagram of CRO	559
9.5	Cathode Ray Tube	560
9.6	Components of CRO	564
9.7	Applications of Oscilloscope	572
9.8	Time Base Generator or Sweep	575
9.9	Introduction to Multimeter	577
9.10	Digital Voltmeter	579
	<i>Solved Examples</i>	582
	<i>Self Test</i>	584
	Index	585-586